

Computer Organization and Architecture

Module 5

Prof. Indranil Sengupta

Dr. Sarani Bhattacharya

Department of Computer Science and Engineering

IIT Kharagpur

Multiplication

Multiplication of Unsigned Numbers

- Multiplication requires substantially more hardware than addition.
- Multiplication of two n -bit number generates a $2n$ -bit product.
- We can use shift-and-add method.
 - Repeated additions of shifted versions of the multiplicand.

[illegible]


A General Case

$$\begin{array}{cccc}
 & & \mathbf{A_3} & \mathbf{A_2} & \mathbf{A_1} & \mathbf{A_0} \\
 & & \mathbf{B_3} & \mathbf{B_2} & \mathbf{B_1} & \mathbf{B_0} \\
 \hline
 & & \mathbf{A_3B_0} & \mathbf{A_2B_0} & \mathbf{A_1B_0} & \mathbf{A_0B_0} \\
 & \mathbf{A_3B_1} & \mathbf{A_2B_1} & \mathbf{A_1B_1} & \mathbf{A_0B_1} & \\
 & \mathbf{A_3B_2} & \mathbf{A_2B_2} & \mathbf{A_1B_2} & \mathbf{A_0B_2} & \\
 \mathbf{A_3B_3} & \mathbf{A_2B_3} & \mathbf{A_1B_3} & \mathbf{A_0B_3} & &
 \end{array}$$


- Each A_iB_j is called a partial product.
- Generating the partial products is easy.
 - Requires just an AND gate for each partial product.
- Adding all the n -bit partial products in hardware is more difficult.

Design of a Combinational Array Multiplier

 - We can directly map the multiplication process as discussed to hardware.
 - We use an array of cells to generate the partial products.
 - Instead of adding the partial products at the end, we add the partial products at every stage of the multiplication.
- The required multiplication cell is as shown.
 - Combines capabilities of partial product generation and also addition of partial products.



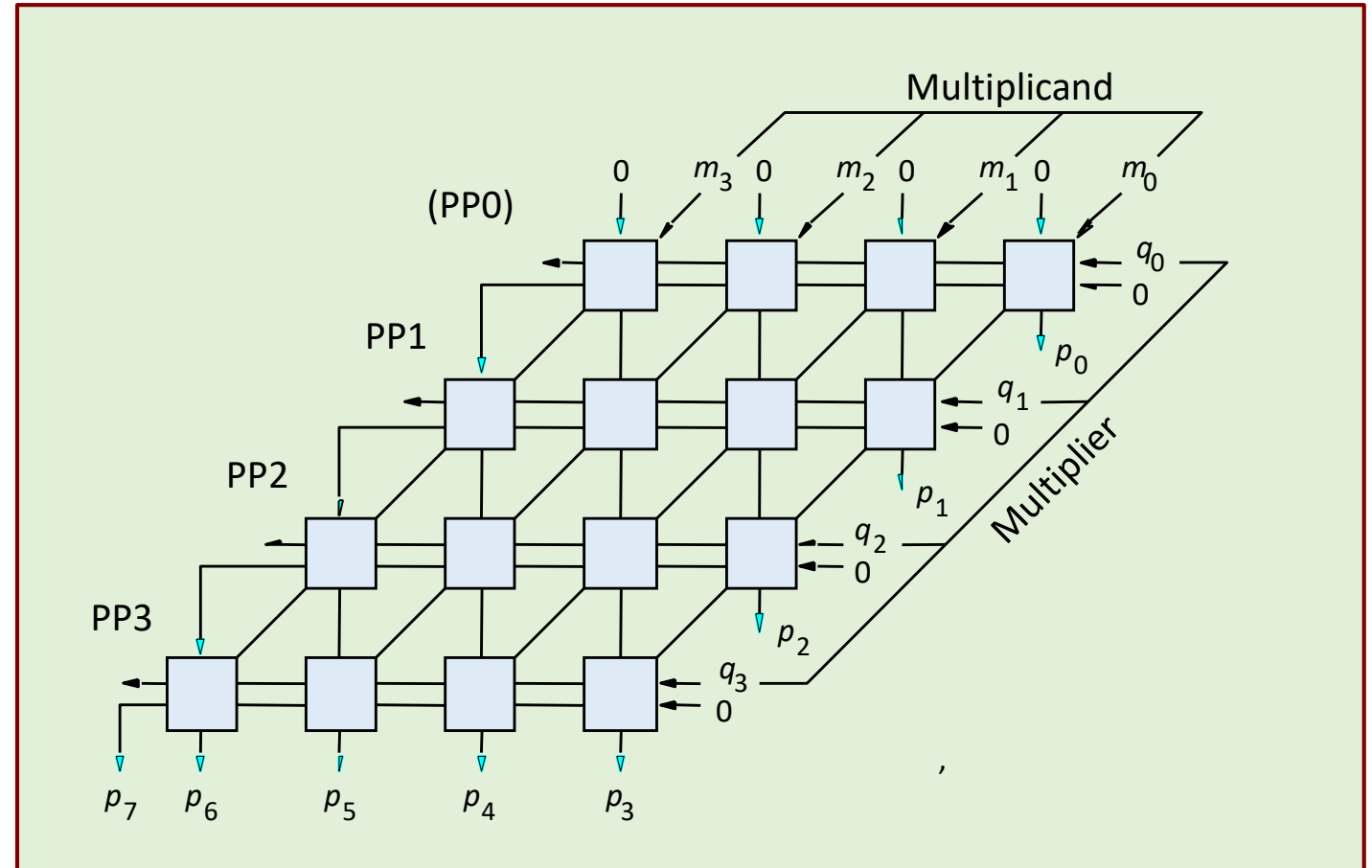- Extremely inefficient, and requires very large amount of hardware.
- Requires n^2 multiplication cells for an $n \times n$ multiplier.
- Advantage is that it is very fast.




Product: $p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0$

Unsigned Sequential Multiplication

- Requires much less hardware, but requires several clock cycles to perform multiplication of two n -bit numbers.
 - Typical hardware complexity: $O(n)$.
 - Typical time complexity: $O(n)$.
- In the “*hand multiplication*” that we have seen:
 - If the i -th bit of the multiplier is 1, the multiplicand is shifted left by i bit positions, and added to the partial product.
 - The relative position of the partial products do not change; it is the multiplicand that gets shifted left.

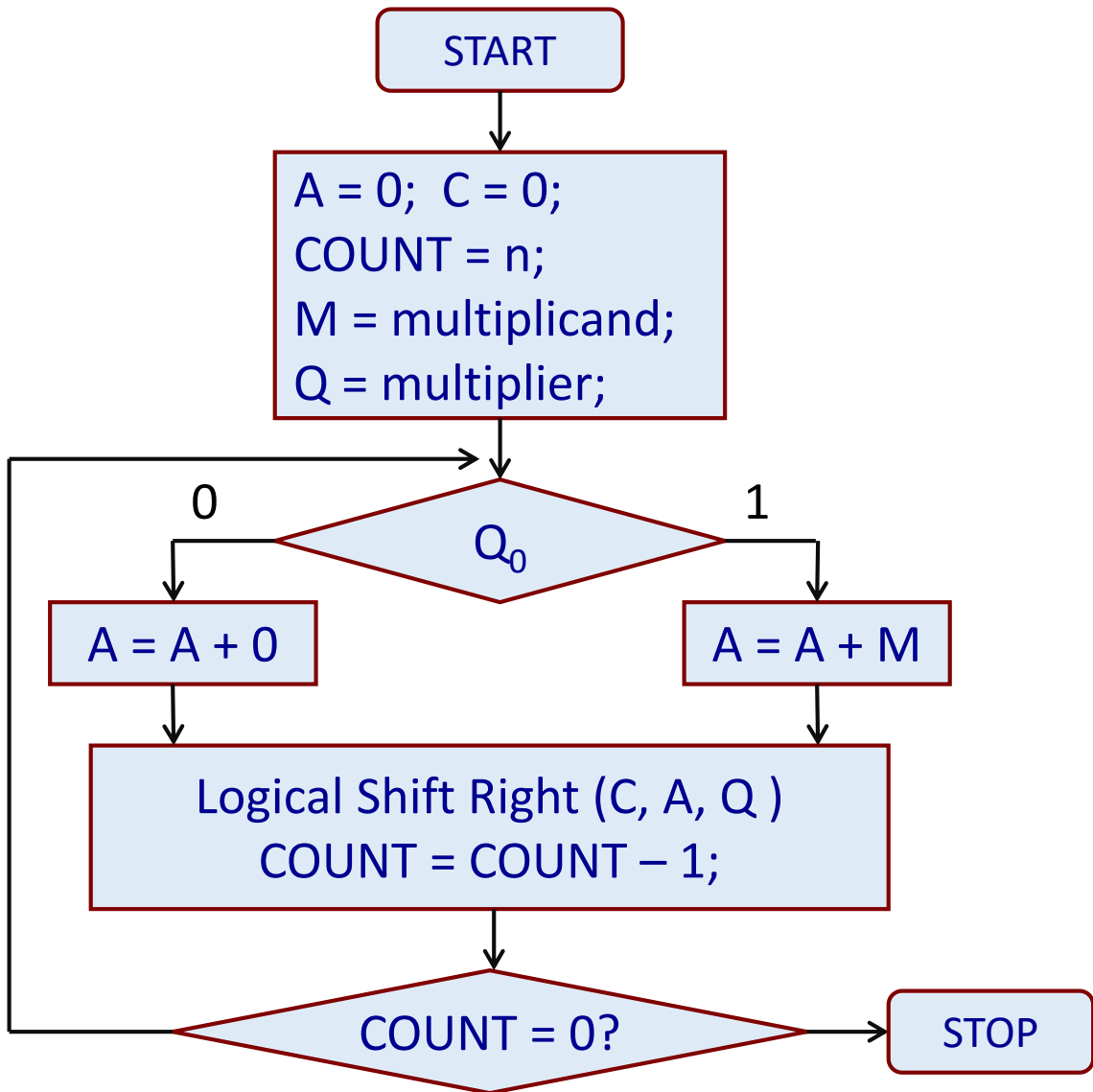- In the “*shift-and-add*” multiplication that we discuss now, we make the following modifications.
 - We do not shift the multiplicand (i.e., keep its position fixed).
 - We right shift an $2n$ -bit partial product at every step.



M: n-bit multiplicand

Q: n-bit multiplier

A: n-bit temporary register

C: 1-bit carry out from adder

Example 1: $(10) \times (13)$

Assume 5-bit numbers.

M: $(0\ 1\ 0\ 1\ 0)_2$

Q: $(0\ 1\ 1\ 0\ 1)_2$

Product = 130

$= (0\ 0\ 1\ 0\ 0\ 0\ 0\ 1\ 0)_2$

C	A	Q		
0	0 0 0 0 0	0 1 1 0 1	Initialization	
0	0 1 0 1 0	0 1 1 0 1	A = A + M	Step 1
0	0 0 1 0 1	0 0 1 1 0	Shift	
0	0 0 1 0 1	0 0 1 1 0	A = A + 0	Step 2
0	0 0 0 1 0	1 0 0 1 1	Shift	
0	0 1 1 0 0	1 0 0 1 1	A = A + M	Step 3
0	0 0 1 1 0	0 1 0 0 1	Shift	
0	1 0 0 0 0	0 1 0 0 1	A = A + M	Step 4
0	0 1 0 0 0	0 0 1 0 0	Shift	
0	0 1 0 0 0	0 0 1 0 0	A = A + 0	Step 5
0	0 0 1 0 0	0 0 0 1 0	Shift	

Example 2: $(29) \times (21)$

Assume 5-bit numbers.

M: $(1\ 1\ 1\ 0\ 1)_2$


Q: $(1\ 0\ 1\ 0\ 1)_2$

Product = 609

$= (1\ 0\ 0\ 1\ 1\ 0\ 0\ 0\ 0\ 1)_2$

C	A	Q		
0	0 0 0 0 0	1 0 1 0 1	Initialization	
0	1 1 1 0 1	1 0 1 0 1	$A = A + M$	Step 1
0	0 1 1 1 0	1 1 0 1 0	Shift	
0	0 1 1 1 0	1 1 0 1 0	$A = A + 0$	Step 2
0	0 0 1 1 1	0 1 1 0 1	Shift	
1	0 0 1 0 0	0 1 1 0 1	$A = A + M$	Step 3
0	1 0 0 1 0	0 0 1 1 0	Shift	
0	1 0 0 1 0	0 0 1 1 0	$A = A + 0$	Step 4
0	0 1 0 0 1	0 0 0 1 1	Shift	
1	0 0 1 1 0	0 0 0 1 1	$A = A + M$	Step 5
0	1 0 0 1 1	0 0 0 0 1	Shift	

Data Path for Shift-and-Add Multiplier

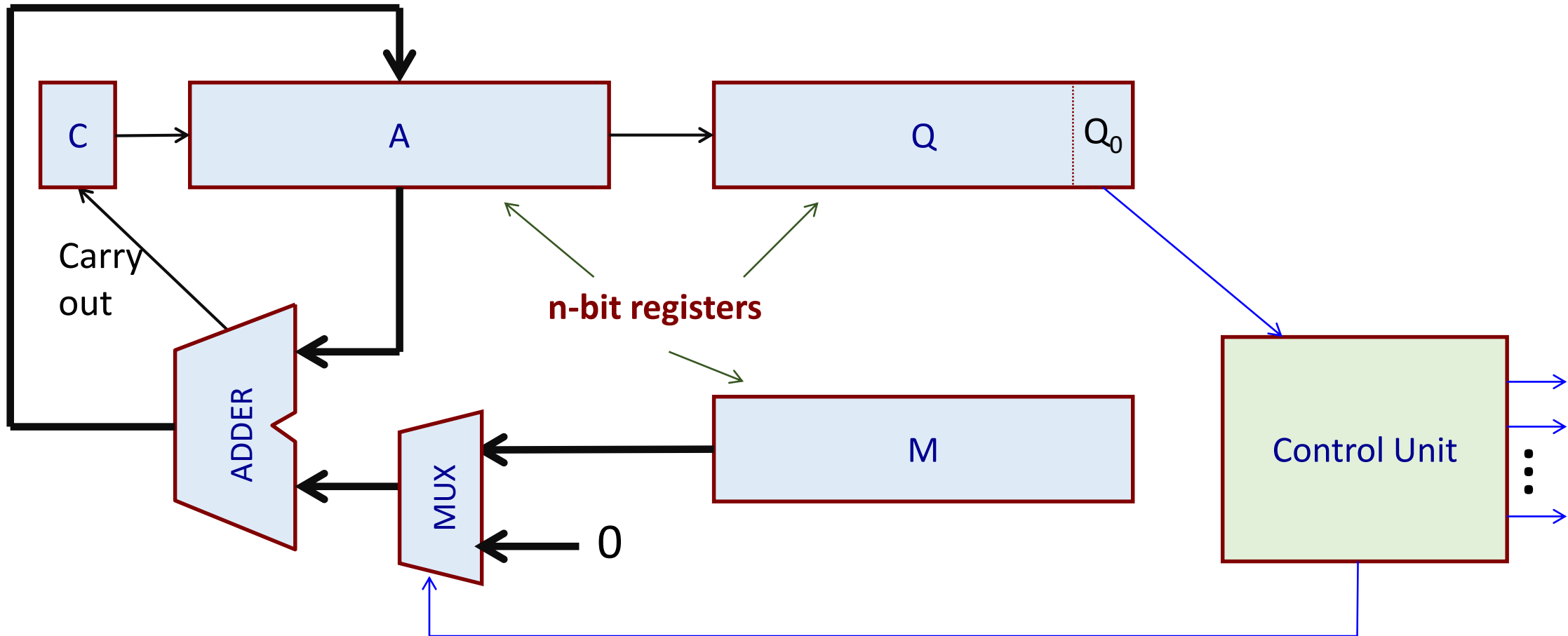

Signed Multiplication

- We can extend the basic shift-and-add multiplication method to handle signed numbers.
- One important difference:
 - Require to sign-extend all the partial products before they are added.
 - Recall that for 2's complement representation, sign extension can be done by replicating the sign bit any number of times.

0101 = 0000 0101 = 0000 0000 0000 0101 = 0000 0000 0000 0000 0000 0000 0000 0101

1011 = 1111 1011 = 1111 1111 1111 1011 = 1111 1111 1111 1111 1111 1111 1111 1011

An Example: 6-bit 2's complement multiplication

Note: For n -bit multiplication, since we are generating a $2n$ -bit product, overflow can never occur.

```

              1 1 0 1 0 1      (-11)
            x 0 1 1 0 1 0      (+26)
            -----
0  0  0  0  0  0  0  0  0  0  0  0
1  1  1  1  1  1  1  0  1  0  1
0  0  0  0  0  0  0  0  0  0
1  1  1  1  1  0  1  0  1
1  1  1  1  0  1  0  1
0  0  0  0  0  0  0
            -----
1  1  1  0  1  1  1  0  0  0  1  0      (-286)

```

Booth's Algorithm for Signed Multiplication

- In the conventional shift-and-add multiplication as discussed, for n -bit multiplication, we iterate n times.
 - Add either 0 or the multiplicand to the $2n$ -bit partial product (depending on the next bit of the multiplier).
 - Shift the $2n$ -bit partial product to the right.
- Essentially we need *n additions and n shift operations*.
- Booth's algorithm is an improvement whereby we can avoid the additions whenever consecutive 0's or 1's are detected in the multiplier.
 - Makes the process faster.


Basic Idea Behind Booth's Algorithm

- We inspect two bits of the multiplier (Q_i, Q_{i-1}) at a time.
 - If the bits are same (00 or 11), we only shift the partial product.
 - If the bits are 01, we do an addition and then shift.
 - If the bits are 10, we do a subtraction and then shift.
- Significantly reduces the number of additions / subtractions.
- Inspecting bit pairs as mentioned can also be expressed in terms of *Booth's Encoding*.
 - Use the symbols +1, -1 and 0 to indicate changes w.r.t. Q_i and Q_{i-1} .
 - $01 \rightarrow +1$, $10 \rightarrow -1$, 00 or $11 \rightarrow 0$.
 - For encoding the least significant bit Q_0 , we assume $Q_{-1} = 0$.

- Examples of Booth encoding:

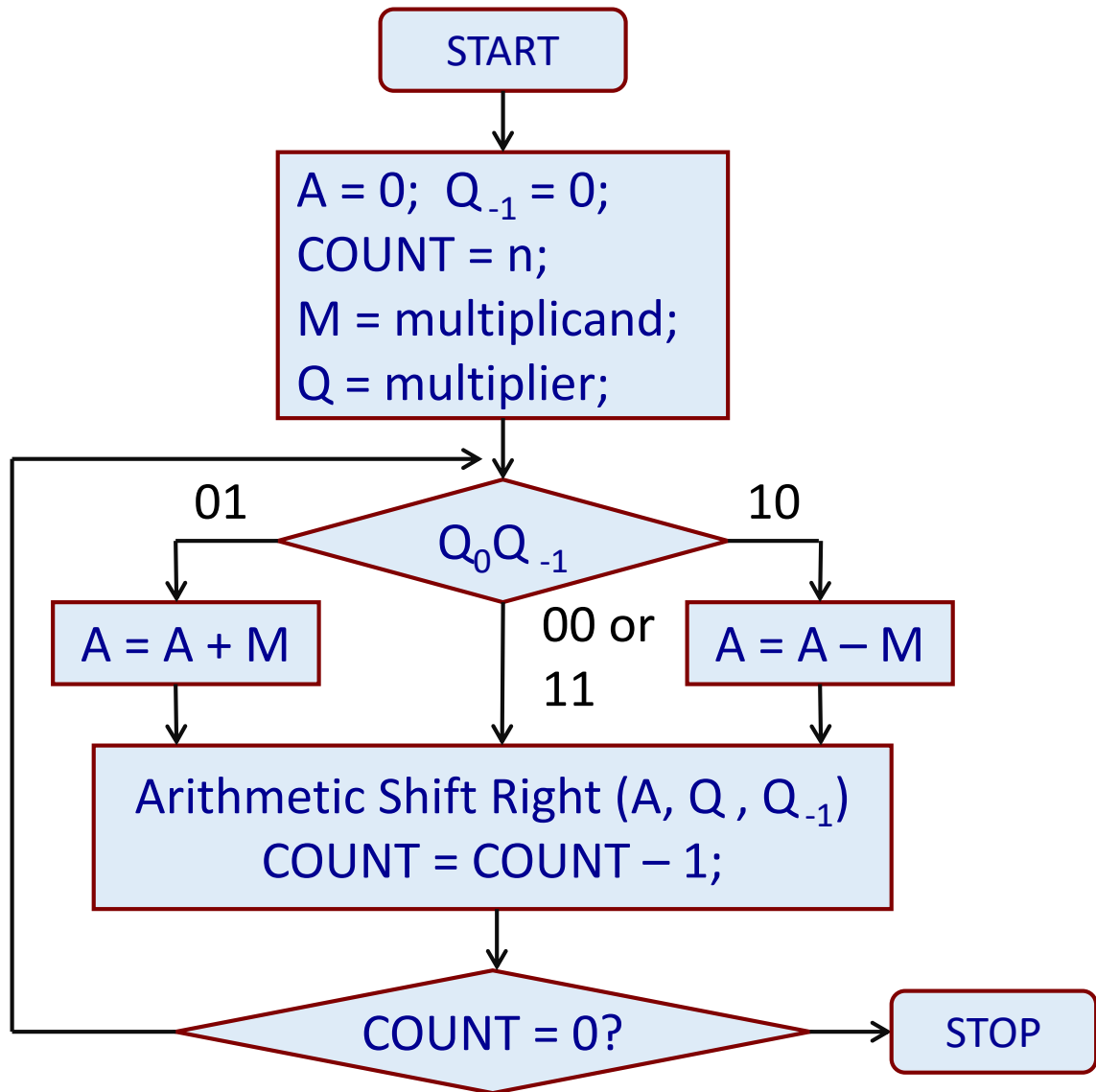a) 0 1 1 1 0 0 0 0 :: +1 0 0 -1 0 0 0 0
b) 0 1 1 1 0 1 1 0 :: +1 0 0 -1 +1 0 -1 0
c) 0 0 0 0 0 1 1 1 :: 0 0 0 0 +1 0 0 -1
d) 0 1 0 1 0 1 0 1 :: +1 -1 +1 -1 +1 -1 +1 -1

- The last example illustrates the *worst case* for Booth's multiplication (alternating 0's and 1's in multiplier).
 - In the illustrations, we shall show the two multiplier bits explicitly instead of showing the encoded digits.



M: n-bit multiplicand

Q: n-bit multiplier

A: n-bit temporary register

Q_{-1} : 1-bit flip-flop

**Skips over consecutive 0's
and 1's of the multiplier Q.**

Example 1: $(-10) \times (13)$

Assume 5-bit numbers.

M: $(1\ 0\ 1\ 1\ 0)_2$

-M: $(0\ 1\ 0\ 1\ 0)_2$

Q: $(0\ 1\ 1\ 0\ 1)_2$

Product = -130

$= (1\ 1\ 0\ 1\ 1\ 1\ 1\ 1\ 0)_2$

A	Q	Q ₋₁	
0 0 0 0 0	0 1 1 0	1 0	Initialization

0 1 0 1 0	0 1 1 0	1 0	A = A - M
0 0 1 0 1	0 0 1 1	0 1	Shift

Step 1

1 1 0 1 1	0 0 1 1	0 1	A = A + M
1 1 1 0 1	1 0 0 1	1 0	Shift

Step 2

0 0 1 1 1	1 0 0 1	1 0	A = A - M
0 0 0 1 1	1 1 0 0	1 1	Shift

Step 3

0 0 0 0 1	1 1 1 1	0 1	Shift
-----------	---------	-----	-------

Step 4

1 0 1 1 1	1 1 1 0	0	A = A + M
1 1 0 1 1	1 1 1 1	0	Shift

Step 5

Example 2:

$(-31) \times (28)$

Assume 6-bit
numbers.

M: $(1\ 0\ 0\ 0\ 0\ 1)_2$

-M: $(0\ 1\ 1\ 1\ 1\ 1)_2$

Q: $(0\ 1\ 1\ 1\ 0\ 0)_2$

Product = -868


= $(1\ 1\ 0\ 0\ 1\ 0$

$0\ 1\ 1\ 1\ 0\ 0)_2$

A	Q	Q ₋₁		
0 0 0 0 0 0	0 1 1 1 0	0 0	Initialization	
0 0 0 0 0 0	0 0 1 1 1	0 0	Shift	Step 1
0 0 0 0 0 0	0 0 0 1 1	1 0	Shift	Step 2
0 1 1 1 1 1	0 0 0 1 1	1 0	A = A - M	Step 3
0 0 1 1 1 1	1 0 0 0 1	1 1	Shift	
0 0 0 1 1 1	1 1 0 0 0	1 1	Shift	Step 4
0 0 0 0 1 1	1 1 1 0 0	0 1	Shift	Step 5
1 0 0 1 0 0	1 1 1 0 0 0	1	A = A + M	Step 6
1 1 0 0 1 0	0 1 1 1 0 0	0	Shift	

Data Path for Booth's Algorithm

Arithmetic
shift right

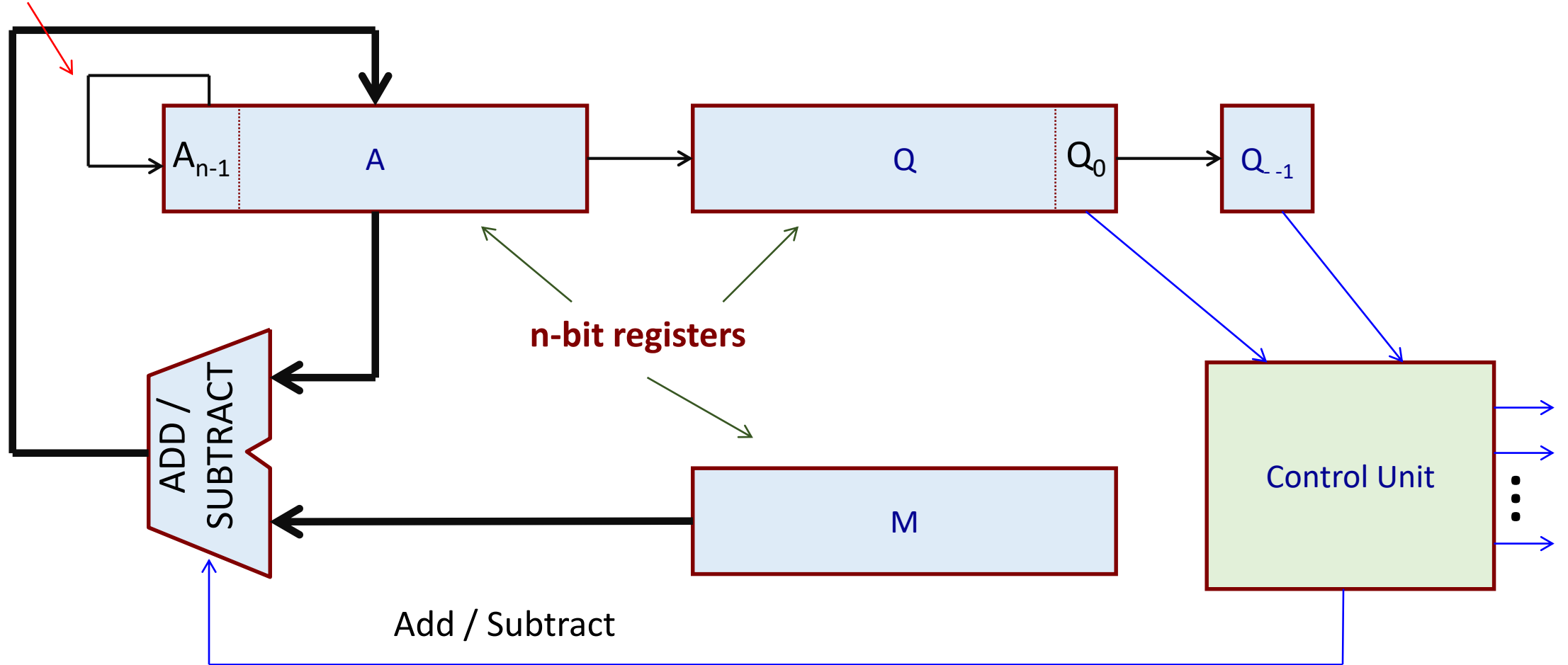

Design of Fast Multiplier

a) Bit-Pair Recoding of Booth's Multiplication

- A technique that halves the maximum number of summands; derived directly from the Booth's algorithm.
- If we group the Booth-coded multiplier digits in pairs, we observe:
 - (+1, -1): $(+1, -1) * M = 2 * M - M = M$
 - (0, +1): $(0, +1) * M = M$
- We need a single addition instead of a pair of addition & subtraction.
 - Other similar rules can be framed.
 - Shown on next slide.

Original Booth-coded Pair	Equivalent Recoded Pair
(+1, 0)	(0, +2)
(-1, +1)	(0, -1)
(0, 0)	(0, 0)
(0, 1)	(0, 1)
(+1, 1)	--
(+1, -1)	(0, +1)
(-1, 0)	(0, -2)

- Every equivalent recoded pair has at least one 0.
- Worst-case number of additions or subtractions is 50% of the number of multiplier bits.
- Reduces the worst-case time required for multiplication.

Example: (+13) X (-22) in 6-bits.

Original:	Multiplier	--	1	0	1	0	1	0
Booth:	Multiplier	--	-1	+1	-1	+1	-1	0
Recoded:	Multiplier	--	0	-1	0	-1	0	-2

			0	0	1	1	0	1	
	.	-1	.	-1	.	-2			

1	1	1	1	1	1	1	0	0	1
1	1	1	1	1	1	0	0	1	1
1	1	1	1	0	0	1	1		


1	1	0	1	1	1	1	0	0	0

- M = 001101 (+13)
- -1 * M = 110011
- -2 * M = 100110

b) Carry Save Multiplier

- We have seen earlier how carry save adders (CSA) can be used to add several numbers with carry propagation only in the last stage.
- The partial products can be generated in parallel using n^2 AND gates.
- The n partial products can then be added using a CSA tree.
- Instead of letting the carries ripple through during addition, we *save* them and feed it to the next row, at the correct weight positions.

4 x 4 Carry Save Multiplier

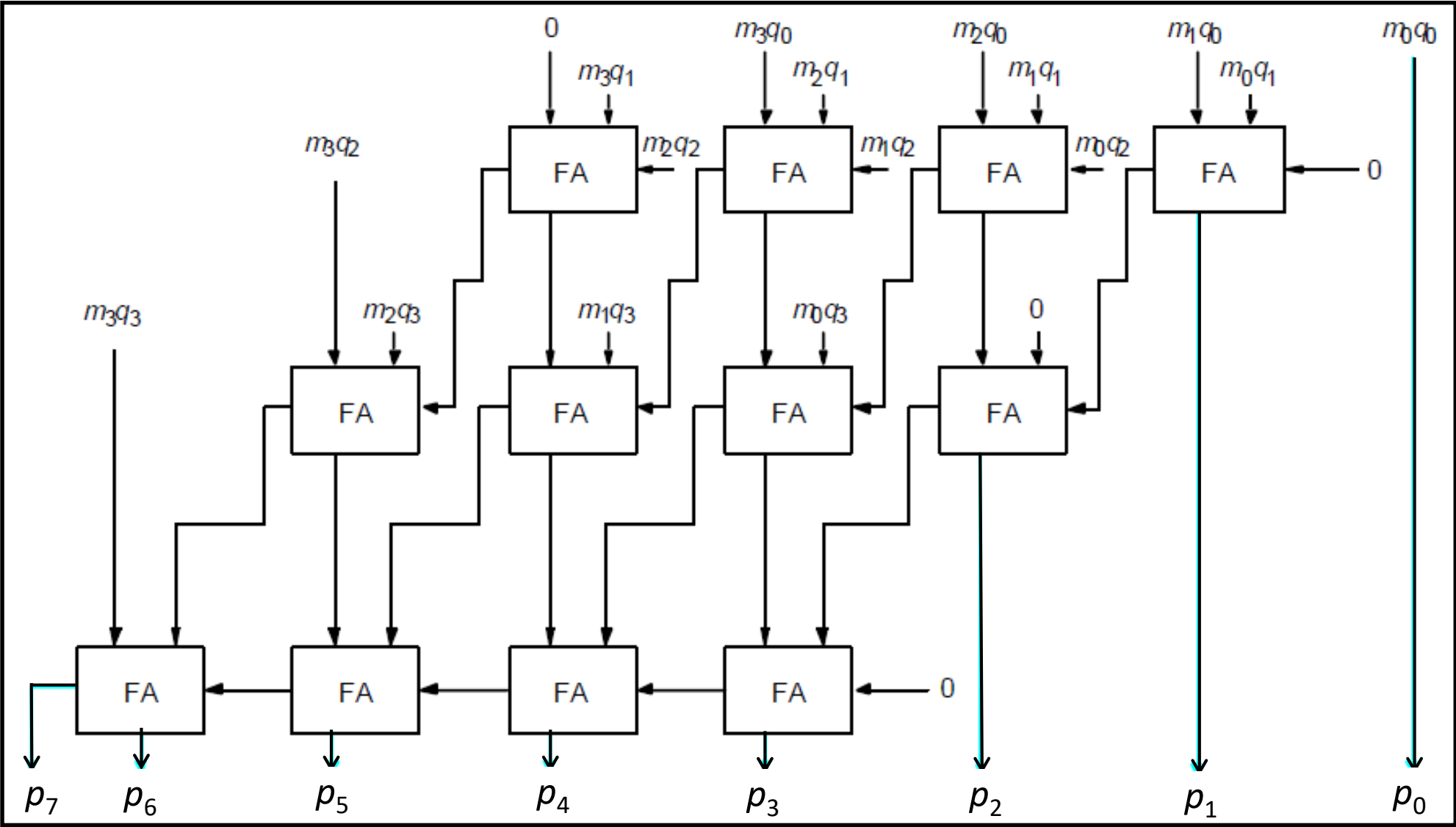

- **Wallace Tree Multiplier**

- A Wallace tree is a circuit that reduces the problem of summing n n -bit numbers to the problem of summing two $\Theta(n)$ -bit numbers.
- It uses $n/3$ (floor of) carry-save adders in parallel to convert the sum of n numbers to the sum of $2n/3$ (ceiling of) numbers.
- It then recursively constructs a Wallace tree on the $2n/3$ (ceiling of) resulting numbers.
- The set of numbers is progressively reduced until there are only two numbers left.
- By performing many carry-save additions in parallel, Wallace trees allow two n -bit numbers to be multiplied in $\Theta(\log_2 n)$ time using a circuit of size $\Theta(n^2)$.

- The figure shows a Wallace tree that adds 8 partial products $m^{(0)}$, $m^{(1)}$, ..., $m^{(7)}$.
- The partial product $m^{(i)}$ consists of $(n+i)$ bits.
- Each line represents an entire number – the label of an edge indicates the number of bits.
- The carry-lookahead adder at the bottom adds a $(2n-1)$ -bit number to a $2n$ -bit number to give the $2n$ -bit product.

