

Blocking and Non-blocking Assignments

Introduction

- Sequential statements within procedural blocks (“always” and “initial”) can use two types of assignments:
 - a) Blocking assignment
 - Uses the ‘=’ operator
 - b) Non-blocking assignment
 - Uses the ‘<=’ operator

Blocking Assignment (using '=')

- Most commonly used type.
- The target of assignment gets updated before the next sequential statement in the procedural block is executed.
- A statement using blocking assignment blocks the execution of the statements following it, until it gets completed.
- Recommended style for modeling combinational logic.

Non-Blocking Assignment (using ' \leq ')

- The assignment to the target gets scheduled for the end of the simulation cycle.
 - Normally occurs at the end of the sequential block.
 - Statements subsequent to the instruction under consideration are not blocked by the assignment.
- Recommended style for modeling sequential logic.
 - Can be used to assign several 'reg' type variables synchronously, under the control of a common clock.

Some Rules to be Followed

- Verilog synthesizer ignores the delays specified in a procedural assignment statement.
 - May lead to functional mismatch between the design model and the synthesized netlist.
- A variable cannot appear as the target of both a blocking and a non-blocking assignment.
 - Following is not permissible:

```
value = value + 1;  
value <= init;
```

```
// Up-down counter (synchronous clear)

module counter (mode, clr, ld, d_in, clk, count);
    input mode, clr, ld, clk;
    input [0:7] d_in;
    output [0:7] count;
    reg [0:7] count;
    always @(posedge clk)
        if (ld)
            count <= d_in;
        else if (clr)
            count <= 0;
        else if (mode)
            count <= count + 1;
        else
            count <= count - 1;
endmodule
```

```
// Parameterized design:: an N-bit counter

module counter (clear, clock, count);
    parameter N = 7;
    input  clear, clock;
    output [0:N] count;
    reg    [0:N] count;

    always @(negedge clock)
        if (clear)
            count <= 0;
        else
            count <= count + 1;
endmodule
```

Example: Ring Counter

```
module ring_counter (clk, init, count);  
    input  clk, init;  
    output [7:0] count;  
    reg [7:0] count;  
    always @(posedge clk)  
    begin  
        if (init)  
            count = 8'b10000000;  
        else begin  
            count    = count << 1;  
            count[0] = count[7];  
        end  
    end  
endmodule
```


Example: Ring Counter (Modified version 1)

```
module ring_counter (clk, init, count);  
    input  clk, init;  
    output [7:0] count;  
    reg [7:0] count;  
    always @(posedge clk)  
    begin  
        if (init)  
            count = 8'b10000000;  
        else begin  
            count    <= count << 1;  
            count[0] <= count[7];  
        end  
    end  
end  
endmodule
```

Example: Ring Counter (Modified version 2)

```
module ring_counter (clk, init, count);  
    input  clk, init;  
    output [7:0] count;  
    reg [7:0] count;  
    always @(posedge clk)  
    begin  
        if (init)  
            count = 8'b10000000;  
        else begin  
            count = {count[6:0], count[7]};  
        end  
    end  
endmodule
```

About “Loop” Statements

- Verilog supports four types of loops:
 - ‘while’ loop
 - ‘for’ loop
 - ‘forever’ loop
 - ‘repeat’ loop
- Many Verilog synthesizers supports only ‘for’ loop for synthesis:
 - Loop bound must evaluate to a constant.
 - Implemented by unrolling the ‘for’ loop, and replicating the statements.

Modeling Memory

- Synthesis tools are usually not very efficient in synthesizing memory.
 - Best modeled as a component.
 - Instantiated in a design.
- Implementing memory as a two-dimensional register file is inefficient.


```
module memory_example (en, clk, adbus, dbus, rw);  
    parameter N = 16;  
    input  en, rw, clk;  
    input  [N-1:0] adbus;  
    output [N-1:0] dbus;  
  
    .....  
    ROM  Mem1  (clk, en, rw, adbus, dbus);  
  
    .....  
endmodule
```

Modeling Finite State Machines


Introduction

- Two types of FSMs:

a) Moore Machine

 


b) Mealy Machine

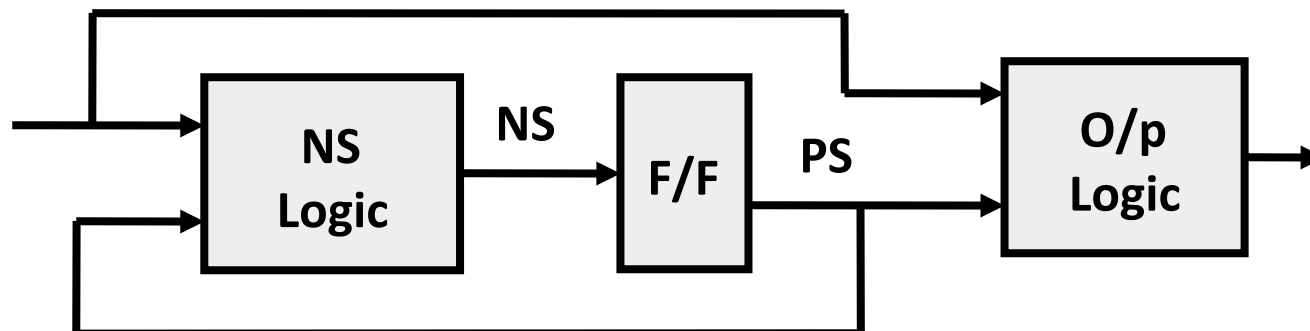

Moore Machine: Example 1

 - Traffic Light Controller
 - Simplifying assumptions made
 - Three lights only (RED, GREEN, YELLOW)
 - The lights glow cyclically at a fixed rate
 - Say, 10 seconds each
 - The circuit will be driven by a clock of appropriate frequency




```

module traffic_light (clk, light);
input  clk;
output [0:2] light;      reg  [0:2] light;
parameter  S0=0, S1=1, S2=2;
parameter  RED=3'b100, GREEN=3'b010, YELLOW=3'b001;
reg [0:1]  state;
always @(posedge clk)
    case (state)
        S0:  begin          // S0 means RED
                    light  <=  YELLOW;
                    state  <=  S1;
                end
        S1:  begin          // S1 means YELLOW
                    light  <=  GREEN;
                    state  <=  S2;
                end
        S2:  begin          // S2 means GREEN
                    light  <=  RED;
                    state  <=  S0;
                end
    end
end

```

```

                                default: begin
                                                light  <=  RED;
                                                state  <=  S0;
                                end
                                endcase
endmodule

```

- Comment on the solution
 - Five flip-flops are synthesized
 - Two for 'state'
 - Three for 'light' (outputs are also latched into flip-flops)
 - If we want non-latched outputs, we have to modify the Verilog code.
 - Assignment to 'light' made in a separate 'always' block.
 - Use blocking assignment.



```

module  traffic_light_nonlatched_op  (clk, light);
    input  clk;
    output [0:2] light;      reg  [0:2] light;
    parameter  S0=0, S1=1, S2=2;
    parameter  RED=3'b100, GREEN=3'b010, YELLOW=3'b001;
    reg [0:1]  state;
    always  @(posedge clk)
        case (state)
            S0:      state  <=  S1;
            S1:      state  <=  S2;
            S2:      state  <=  S0;
            default:  state  <=  S0;
        endcase
    always  @(state)
        case (state)
            S0:      light  =  RED;
            S1:      light  =  YELLOW;
            S2:      light  =  GREEN;
            default:  light  =  RED;
        endcase
endmodule

```

Moore Machine: Example 2

- Serial parity detector

  

```

module parity_gen (x, clk, z);
    input  x, clk;
    output z;      reg  z;
    reg  even_odd;    // The machine state
    parameter  EVEN=0, ODD=1;


    always @(posedge clk)
        case (even_odd)
            EVEN: begin
                    z  <=  x ? 1 : 0;
                    even_odd  <=  x ? ODD : EVEN;
                end
            ODD:  begin
                    z  <=  x ? 0 : 1;
                    even_odd  <=  x ? EVEN : ODD;
                end
        endcase
endmodule

```

- If no output latches need to be synthesized, we can follow the principle shown in the last example

Mealy Machine: Example

 - Sequence detector for the pattern '0110'.



```

module seq_detector (x, clk, z)
  input  x, clk;
  output z;          reg  z;
  parameter S0=0, S1=1, S2=2, S3=3;
  reg [0:1] PS, NS;

  always @(posedge clk)
    PS <= NS;

  always @ (PS or x)
    case (PS)
      S0: begin
          z  = x ? 0 : 0;
          NS = x ? S0 : S1;
        end;
      S1: begin
          z  = x ? 0 : 0;
          NS = x ? S2 : S1;
        end;
    endcase
endmodule


```

```

      S2: begin
          z  = x ? 0 : 0;
          NS = x ? S3 : S2;
        end;
      S3: begin
          z  = x ? 0 : 1;
          NS = x ? S0 : S3;
        end;
    endcase
endmodule

```

Example with Multiple Modules

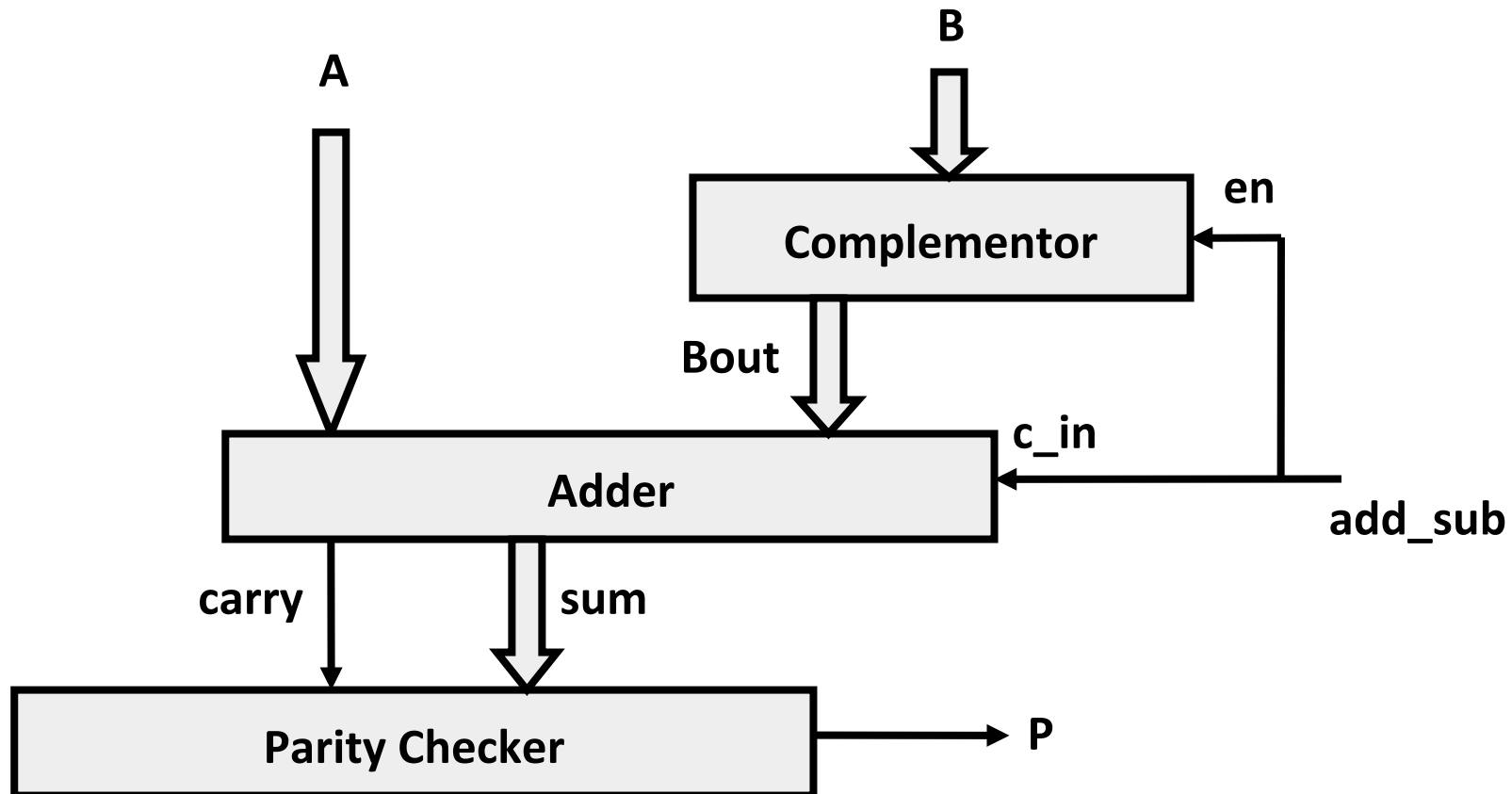


```

module complementor (Y, X, comp);
    input [7:0] X;
    input comp;
    output [7:0] Y;
    reg [7:0] Y;

    always @(X or comp)
        if (comp)
            Y = ~X;
        else
            Y = X;
endmodule

```

```

module adder (sum, cy_out, in1, in2, cy_in);
    input [7:0] in1, in2;
    input cy_in;
    output [7:0] sum;      reg [7:0] sum;
    output cy_out;        reg cy_out;

    always @(in1 or in2 or cy_in)
        {cy_out, sum} = in1 + in2 + cy_in;
endmodule

```

```

module parity_checker (out_par, in_word);
    input [8:0] in_word;
    output out_par;

    always @(in_word)
        out_par = ^(in_word);
endmodule

```

```
// Top level module
module  add_sub_parity (p, a, b, add_sub);
    input [7:0] a, b;
    input  add_sub;           // 0 for add, 1 for subtract
    output p;                // parity of the result
    wire [7:0] Bout, sum;
    wire  carry;

    complementor    M1 (Bout, B, add_sub);
    adder           M2 (sum, carry, A, Bout, add_sub);
    parity_checker  M3 (p, {carry, sum});
endmodule
```