

# Group -8

## Assignment 3

Bratin Mondal (21CS10016)

Somya Kumar (21CS30050)

Submitted on: August 24th, 2023

## GCD Calculation

### The Algorithm:

#### 1. The pseudocode:

```
int A, int B;

while( A != 0 & B != 0 )
{
    if(A == 0)
        return B;
    if(B == 0)
        return A;
    if(A > B)
        A = A - B
    else
        B = B - A
}
```

The GCD module calculates the Greatest Common Divisor of two positive integers.

#### 2. The Design:

The GCD module has the following parameters:

1. input wire rst: Checks if the module is to be reset from the beginning. rst is set to 1 for the first iteration of the loop and set to 0 for further iterations of the loop.
2. Input wire clk: It is the clock pulse which is sent to the module
3. input [7:0] A: 8 bit number A as input
4. input [7:0] B: 8 bit number B as input
5. output reg [7:0] result: The result of the module

The module contains the following variables:

1. reg\_A: It stores the intermediate value of A in the calculation
2. reg\_B: It stores the intermediate value of A in the calculation
3. reg\_result: It stores the intermediate value of result in the calculation

### 3. Working:

The workings of the module are as follows:


In each clock cycle:

1. If reset mode is on, we do the following. This particular line of the check condition in line 15 will be implemented through a **comparator** in the circuit.
  - a. Load A into reg\_A
  - b. Load B to reg\_B
  - c. Load 0 to reg\_result
  - d. Load 0 to result
2. Else if reset mode is off, we do as follows.
  - a. If the value in reg\_A is 0, then we set the value of result to reg\_B. This particular line of the check condition in line 22 will be implemented through a **comparator** in circuit.
  - b. Else if the value in reg\_B is 0 then we set the value of result to reg\_A. This particular line of the check condition in line 26 will be implemented through a **comparator** in circuit.
  - c. Else if the value of reg\_A is greater than reg\_B, we set value of reg\_A to reg\_A-reg\_B. This particular line of

the check condition in line 32 will be implemented through a **comparator** in circuit.

- d. Else if the value of reg\_B is greater than reg\_A, we set value of reg\_B to reg\_B-reg\_A.

#### 4. Structure:

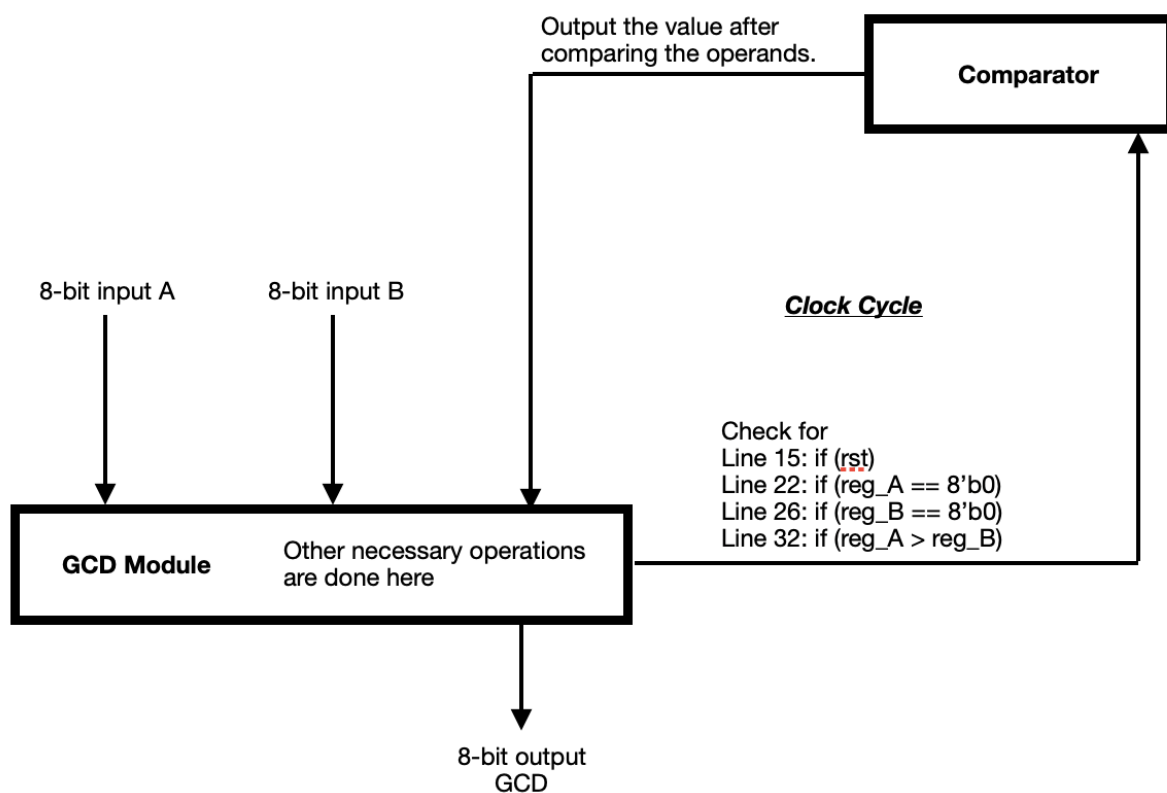

#### The Test Bench:

The test bench we submitted calculates the GCD for 120 and 165

#### Working:

We keep toggling the clock after every 5 time units.  
The test bench works as follows.

1. Initialize the clock with 0
2. Initialize rst with 1
3. Initialize A with 120
4. Initialize B with 165
5. Wait 15 time units for reset
6. set rst to 0 for further iterations of loop
7. Wait for the gcd calculation to complete
8. Output the GCD value